

[Total No. of Questions - 9] [Total No. of Printed Pages - 2]

May-24-0363

EC-101 (Fundamentals of Electronics Engineering)

B.Tech. 2nd (CBCS)

Time : 3 Hours

Max. Marks : 60

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

**Note :** Attempt five questions in all, selecting one question each from Sections A, B, C and D. Section E is compulsory.

#### SECTION - A

1. (a) Explain the difference between Metal, Insulator and Semiconductor by showing Fermi level. (5)  
(b) Describe the LED and Seven-Segment Display with diagram. (5)
2. Draw and explain the working of Bridge Rectifier. Derive the equation for ripple frequency and efficiency of the bridge rectifier. (10)

#### SECTION - B

3. Explain the Input and Output characteristics of CB and CE configuration of BJT. (10)
4. Draw and explain the working principle of n-Channel JFET with transfer and drain characteristics. (10)

#### SECTION - C

5. Describe the working principle of Oscillator and explain the RC phase shift Oscillator and Wein Bridge Oscillator with diagram. (10)

2

EC-101

6. Explain the linear application of Op-Amp in terms of Inverting, Non-inverting and Differential amplifier. (10)

#### SECTION - D

7. (a) Convert the octal number  $(257.46)_8$  into binary, hexadecimal and decimal numbers. (5)  
(b) Realize NOT gate by using XOR gate. (5)
8. Explain the measurement of Voltage, Phase and Frequency by using CRO. (10)

#### SECTION - E (Compulsory)

9. Write brief answers. All carry equal marks.
  - (i) Realize AND gate using only NOR gate.
  - (ii) What factors affect the gain of the amplifier at high frequencies?
  - (iii) What is the basic concept of operational amplifier?
  - (iv) Explain the Zener Diode as Voltage Regulator with circuit diagram.
  - (v) How is the gate-source diode of a JFET biased?
  - (vi) If the base resistor is very small, then the transistor will operate in which region?
  - (vii) Draw the cross-section of depletion mode and enhancement mode for n-channel MOSFET.
  - (viii) Define beta ratio of Transistor.
  - (ix) Explain the operation of CRO with circuit diagram.
  - (x) Convert the two's complement number  $(1101)_2$  into its decimal equivalent. (10×2=20)